

WANG, Tiffany 260684152

YE, Frank 260689448

GROUP 08 - MacroHard EE

G08 7-SEGMENT DECODER

Introduction

Seven-segment display is a popular way of representing numbers and is used in various scenarios such as clocks, crosswalk countdowns, etc. This lab will mainly transcribe a seven-bits input to a seven-segment display code.

The 7-segment lab component fully coded in VHDL by the authors of this report, Tiffany Wang and Frank Ye.

Introduction	1
VHDL Code	2
Testing	2

1. VHDL Code

The entity `g08_7_segment_decoder` takes in a 4-bits code and a 1-bit input, which determines the mode of the display: '0' corresponds to HEX, and '1' to cards. An intermediate 5-bit vector signal `xcode` merges the code and mode together for easier manipulation later. Each input code is associated to a corresponding 7-segment display output encoding using the With/Select method. This design offers the advantage of an one-to-one mapping between inputs/outputs.

2. Testing

The VHDL code was tested with a simulated waveform. Since the way the With/Select code functions is straightforward, we simply tested the 32 possibilities of the input range to ensure desired behavior, since this component will be reused for the final project.

The simulated waveform is the following:

The results are as expected. Every output corresponds to the 7-segment encoding of the input. However, it is hard to visualize the result simply by comparing bits vectors. Mistake may have occurred when writing out the encoding of the input for example. This is a limitation we currently have for this lab. A better test would be conducted once we receive FPGA board with the actual integrated 7-segment display hardware.