

WANG, Tiffany 260684152

YE, Frank 260689448

GROUP 08 - MacroHard EE

G08 RANDU CIRCUIT

The goal of the lab is to describe a random number generator circuit using VHDL, to be familiar with the use library design entities and to use ROM modules to implement look-up tables. The random number generator circuit will be based off the **linear congruential generator algorithm**:

$$R = \text{mod} (a*SEED + b, c)$$

In the following report, we will present and justify our design through the display of our test results.

TABLE OF CONTENT

Circuit Description	2
VHDL Description	2
Testing	3
Advantages and Limitations	3
References	4

1. Circuit Description

Circuit Function:

As described in the introduction of the report, the goal of the lab is to design a basic random generator circuit based on the algorithm:

$$R = \text{mod}(a * SEED + b, c)$$

where a , b , c are constants, $SEED$ is an arbitrary initial value and R is the random number output. To obtain different values of R , for the same a , b , c parameters one must replace $SEED$ with R and re-compute the output.

The parameters we implemented for this design is based on the IBM RANDU function:

- $a = 65539$
- $b = 0$
- $c = 2^{31}$

2. VHDL Description

The entity `g08_RANDU` takes in a 32-bit input `SEED` that will generate a 32 bit output `SEED`.

The representation of the decimal number 65539 in binary is 10000000000000011, which is $2^{16} + 2^1 + 2^0$. Therefore, the operation of $X * 65539$ can be simply computed through a series of shifts and additions. Namely,


$$X * 65539 = \text{ShiftLeft_16}(X) + \text{ShiftLeft_1}(X) + X$$

For our circuit design, since we set parameter b to 0, the last operation before the final output is to perform a $A \bmod 2^{31}$ calculation. This works out to simply retaining the $N - 31$ MSB, N being the number of input bits in the operation. In this case, $A = X * 65539$ mentioned previously. Thus, we end up with a 32 bit output.

INPUT: seed[31..0]

OUTPUT: rand[31..0]
 
$$\text{rand} = \text{mod}(65539 * \text{seed}, 2^{31})$$



RANDU circuit schematic

3. Testing

Since testing the 2^{32} possible inputs is impractical, the circuit was tested by choosing an initial seed value of 00000000000000000000000000000001, running the simulation, then using the first output as the seed value for the second simulation. The simulation was run 5 times, and the result was verified for every run.

in	> seed	U 1	1	in	> seed	U 65539	65539	in	> seed	U 393225	393225
out	> rand	U 65539	65539	out	> rand	U 393225	393225	out	> rand	S 1769499	1769499
in	> seed	U 1769499	1769499	in	> seed	U 7077969	7077969	in	> seed	U 26542323	26542323
out	> rand	U 7077969	7077969	out	> rand	U 26542323	26542323	out	> rand	U 95552217	95552217

Moreover, due to its poor design, the following equation should hold if the RANDU circuit was designed correctly.

$$\text{mod}(R_n - 6R_{n-1} + 9R_{n-2}, 2^{3l}) = 0$$

We have $(95552217 - 6 * 26542323 + 9 * 7077969) \% 2^{31} = 0 \ \% 2^{31} = 0$

As well, a wrap around of the modulo is expected occur when the seed exceeds 2^{16} , as shown in our test results.

Name	10.0 ns	20.0 ns	30.0 ns	40.0 ns	50.0 ns	60.0 ns	70.0 ns	80.0 ns	90.0 ns	100.0 ns
seed	65530	65531	65532	65533	65534	65535	65536	65537	65538	65539
rand	4294770670	4294836209	4294901748	4294967287	65530	131069	196608	262147	327686	393225

4. Advantages and Limitations

The obvious advantage of this circuit is its simple implementation. The modulo and multiplication circuits required a lot less circuitry due to the fact that for those operations, we could merely match the correct input bits, e.g. when multiplying by a power of 2. The lack of physical shift registers prevents problems such as gate delays and clock implementations. Hence, we were able to write VHDL code to perform all operations using the lpm add modules.

However, due to its simplicity, the numbers generated by this circuit are easily predictable, as indicated by the above equation. Hence, this design could not be used for serious applications.

5. References

- [1] Clark J., *Lab #2 - Combinational Circuit Design with VHDL*, ECSE 323 Digital System Design, Fall 2017
- [2] Altera. LPM Quick Reference Guide, December 1996
- [3] Altera. lpm_add_sub Megafunction User Guide, March 2007
- [4] Altera. lpm_rom Megafunction User Guide, March 2005